



The University of Azad Jammu and Kashmir, Muzaffarabad

Name**Tayyab Hanif**

Course Name	Computer Architecture and Logic Design
Submitted to	Engr. Sidra Rafique
Semester	2nd
Session	2024-2028
Roll No	2024-SE-11
Lab	Open Ended Lab
Submission date	05 September 2025

Task 1: Parity Generator and Checker

1. 4-bit Parity Generator Circuit

- Inputs: A, B, C, D (4-bit data word).
- Output: Parity Bit (P).
- **Even parity rule:** The parity bit is chosen such that the total number of 1's (data bits + parity) is even.

Boolean Equation:

$$P = A \oplus B \oplus C \oplus D$$

2. Implementation

- Use XOR gates in PLA or a digital logic simulator like Electronic Work Bench..
- Connect inputs A, B, C, D \rightarrow XOR chain \rightarrow Output P.

3. Testing the Generator

- Try all 16 combinations of A, B, C, D.
- Verify that $(A \oplus B \oplus C \oplus D) + P$ always gives **even number of 1s**.

4. Parity Checker Circuit

- Inputs: A, B, C, D, and received Parity Bit (P).
- Output: Error signal (E).

Boolean Equation:

$$E = A \oplus B \oplus C \oplus D \oplus P$$

- If $E = 0 \rightarrow$ No error.
- If $E = 1 \rightarrow$ Error detected.

5. Implementation and Testing

- Connect inputs to XOR chain.
- Apply different data with parity bit.
- Check if circuit correctly detects error when a bit flips.

4-bit Parity Generator Circuit

 


Figure 1: When two Switch is OFF and two ON means inputs $(A, B, C, D) = (0, 1, 0, 1)$ then output is 0.


 


Figure 2: When three Switches ON and one OFF means all inputs $(A, B, C, D) = (1, 1, 1, 0)$, then output is 1.

4-bit Parity Generator (Even Parity): -

$$\text{Formula: } P = A \oplus B \oplus C \oplus D$$

A	B	C	D	P (Parity)
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

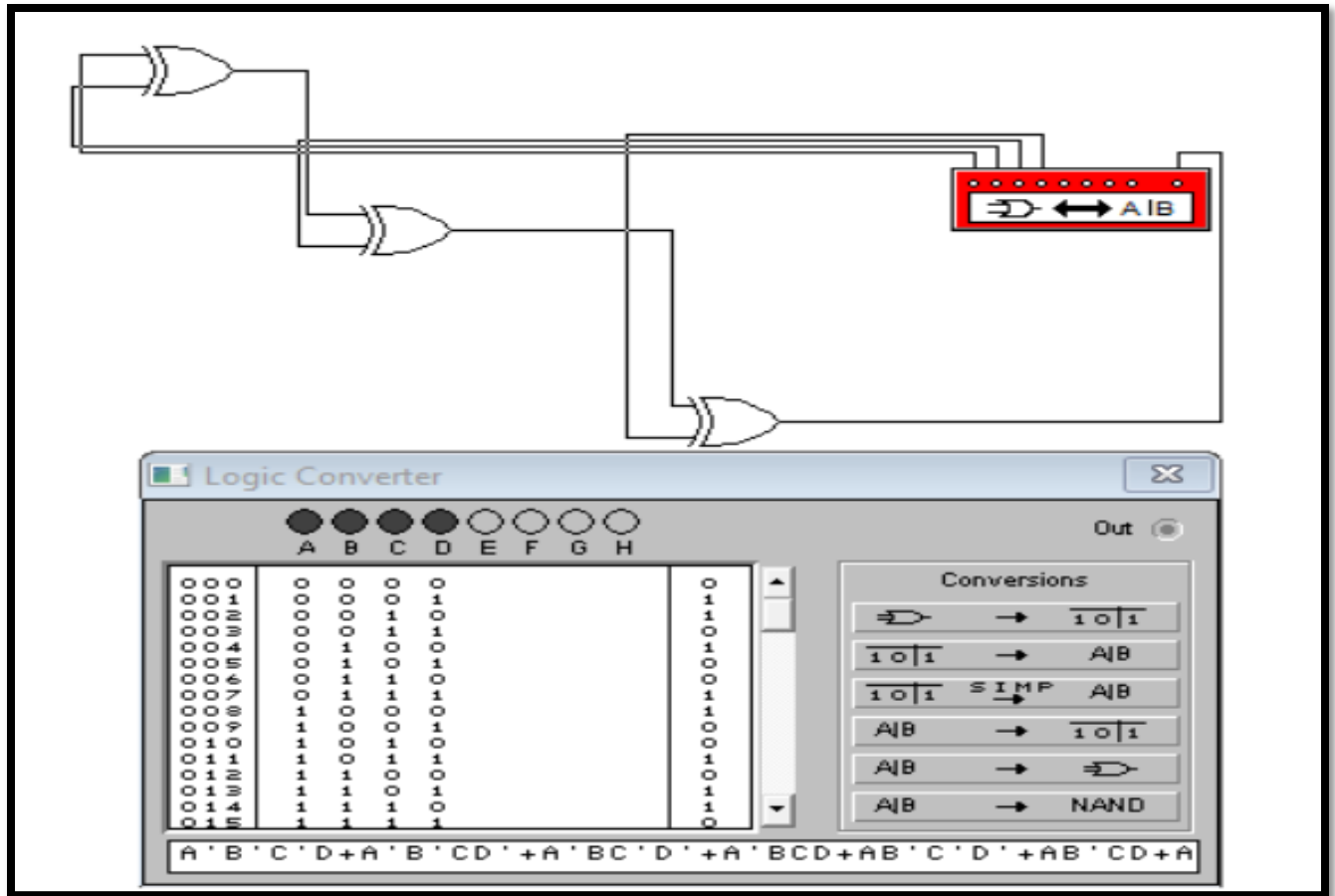

4-bit Parity Checker (Error Detection)

- Inputs: A, B, C, D, and received Parity Bit (P).
- Output: Error signal (E).

Boolean Equation:

$$E=A\oplus B\oplus C\oplus D\oplus P$$

- If $E = 0 \rightarrow$ No error.
- If $E = 1 \rightarrow$ Error detected.

Implementation and Testing

- Connect inputs to XOR chain.
- Apply different data with parity bit.
- Check if circuit correctly detects error when a bit flips.

4-bit Parity Checker (Error Detection)

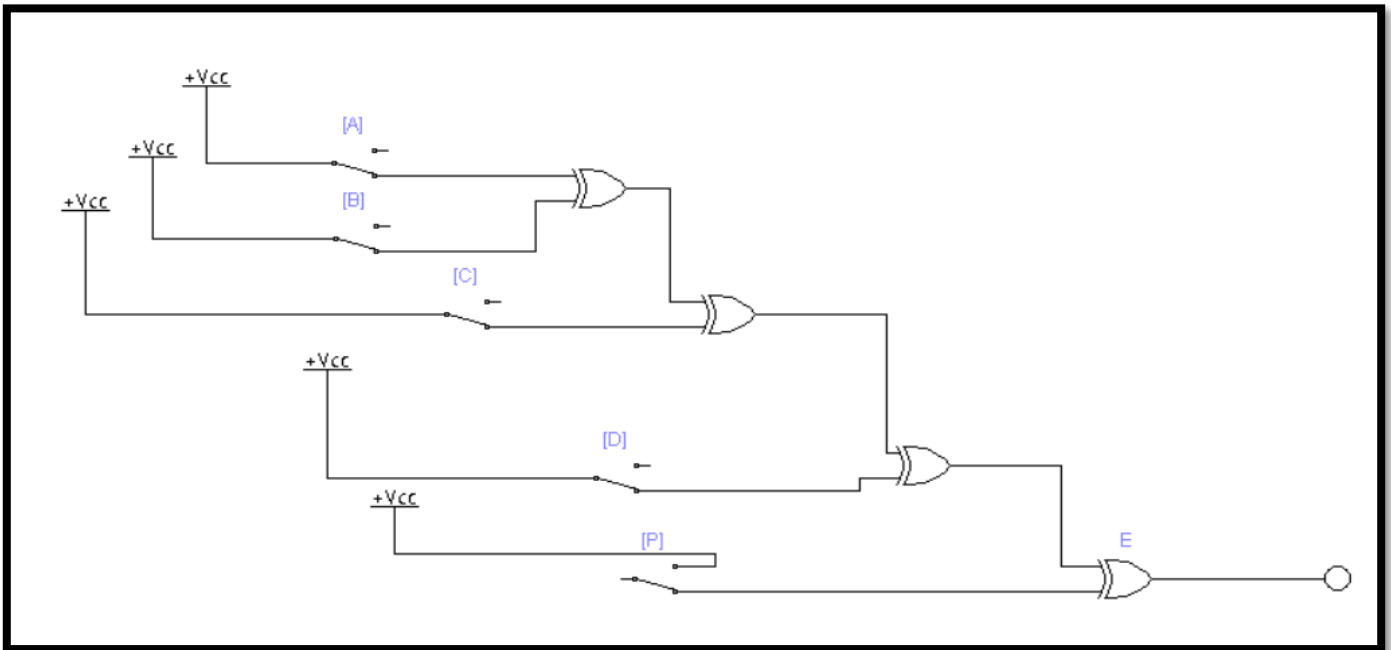


Figure 1 : When four Switches ON and one OFF means all inputs $(A, B, C, D, P) = (1, 1, 1, 1, 0)$, then output is 0.

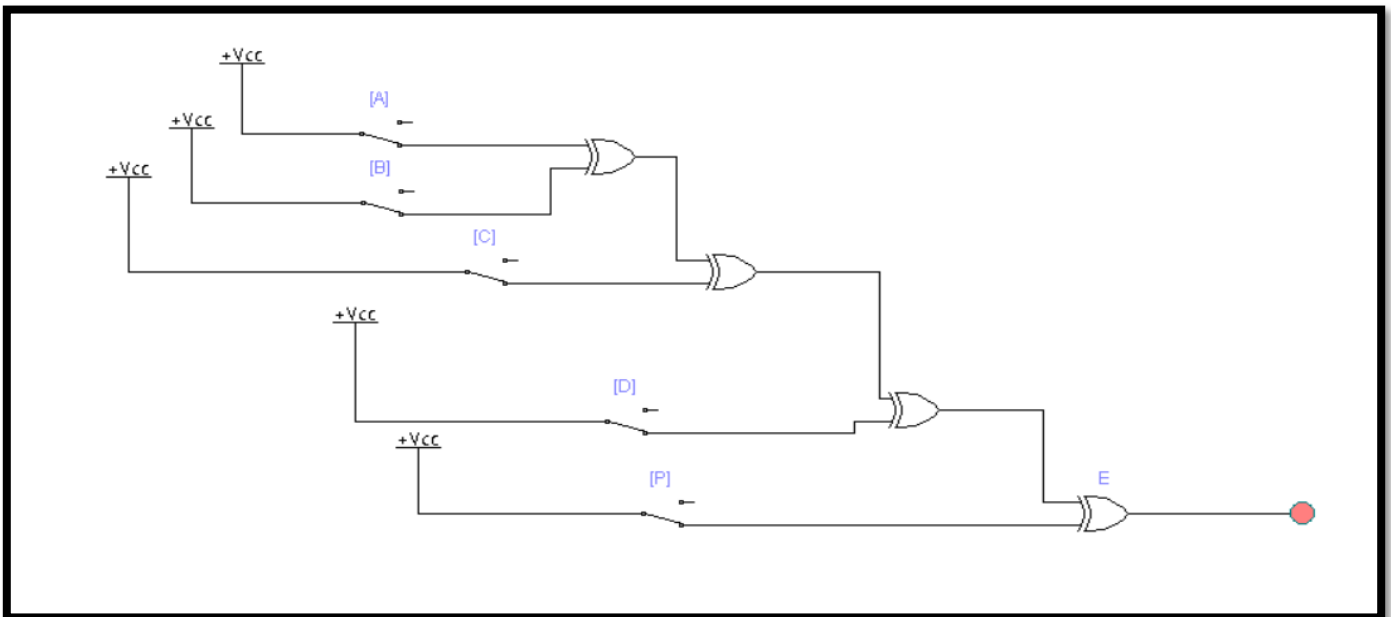


Figure 2: When all Switches ON means all inputs $(A, B, C, D, P) = (1, 1, 1, 1, 1)$, then output is 1

Parity Checker Truth Table

Boolean Equation:

$$E = A \oplus B \oplus C \oplus D \oplus P$$

Inputs: **A, B, C, D, P** → Output: **E (Error)**

A	B	C	D	P (Expected)	E (Output)	Meaning
0	0	0	0	0	0	✓ No error
0	0	0	0	1	1	✗ Error
1	0	1	0	0	0	✓ No error
1	0	1	0	1	1	✗ Error
1	1	1	1	0	0	✓ No error
1	1	1	1	1	1	✗ Error

Task 2: Low-Level Program for Shift Instructions

1. **SHL (Shift Left Logical)** – Multiplies number by 2.
2. **SHR (Shift Right Logical)** – Divides unsigned number by 2.
3. **SAR (Shift Arithmetic Right)** – Divides signed number by 2, keeps sign.
4. **SAL (Shift Arithmetic Left)** – Similar to SHL.

MOV AL, 00001101b ; Load data = 13 (binary)

SHL AL, 1 ; Shift Left → result = 26


SHR AL, 1 ; Shift Right → result = 13

SAR AL, 1 ; Arithmetic Right → sign preserved

SAL AL, 1 ; Arithmetic Left → same as SHL

By using emulator,

Step #01:

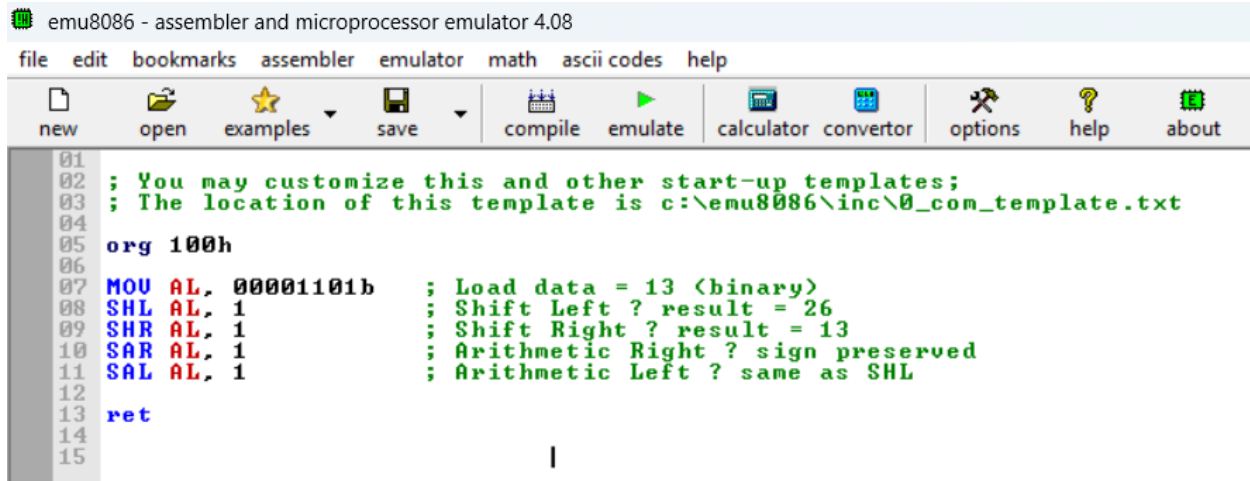


```

01
02 ; You may customize this and other start-up templates;
03 ; The location of this template is c:\emu8086\inc\0_com_template.txt
04
05 org 100h
06
07 MOV AL, 00001101b ; Load data = 13 (binary)
08 SHL AL, 1 ; Shift Left ? result = 26
09 SHR AL, 1 ; Shift Right ? result = 13
10 SAR AL, 1 ; Arithmetic Right ? sign preserved
11 SAL AL, 1 ; Arithmetic Left ? same as SHL
12
13 ret
14
15

```

Result:

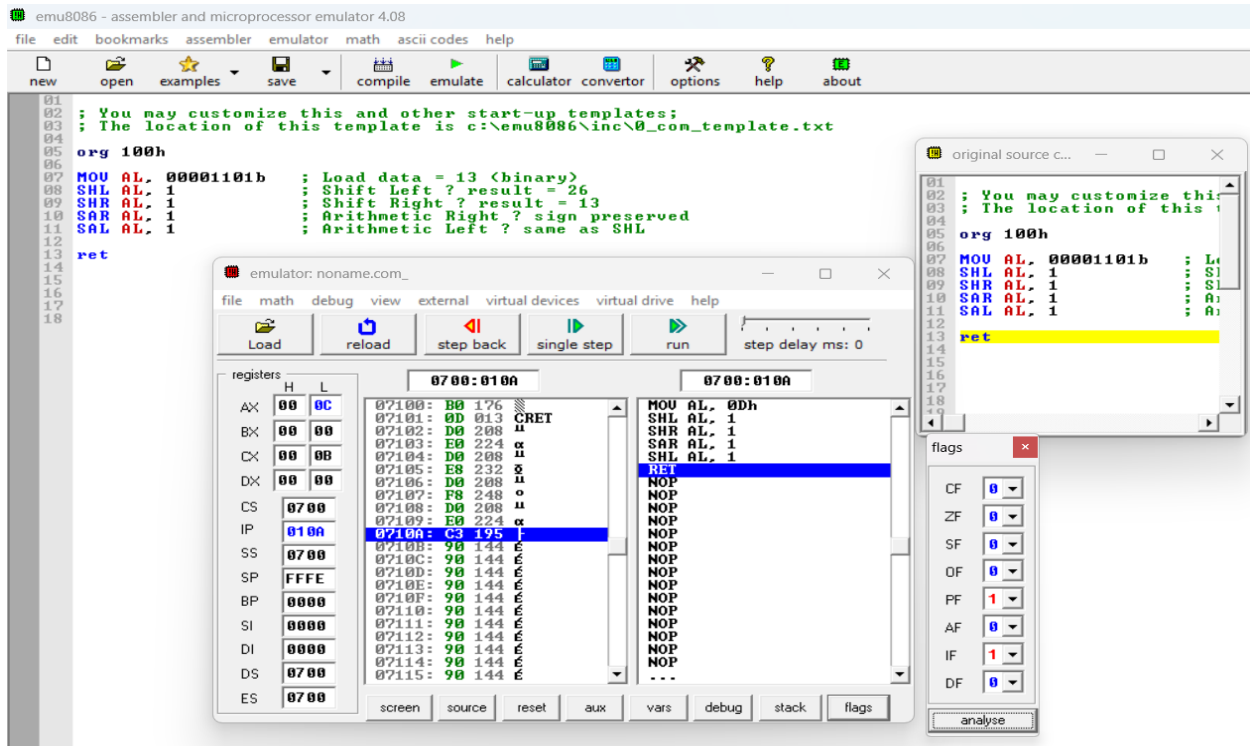

The screenshot shows the emu8086 emulator 4.08 interface. The assembly code from the previous step is loaded and executed. The registers window displays the state of the CPU registers, and the flags window shows the status of the flags.

Registers:

Register	Value
AX	00 0C
BX	00 00
CX	00 00
DX	00 00
CS	0700
IP	010A
SS	0700
SP	FFFE
BP	0000
SI	0000
DI	0000
DS	0700
ES	0700

Flags:

Flag	Value
CF	0
ZF	0
SF	0
OF	0
PF	1
AF	0
IF	1
DF	0

Deliverables

1. Working Circuits

- 4-bit parity generator and checker implemented in simulator.

2. Truth Table & Boolean Equations

A	B	C	D	Parity $P = A \oplus B \oplus C \oplus D$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
...

Boolean Equation:

$$E = A \oplus B \oplus C \oplus D \oplus P$$

3. Summary

- Designed a 4-bit parity generator using XOR gates.
- Verified functionality with truth table and simulation.
- Designed a parity checker for error detection.
- Implemented and tested both circuits in simulator.
- Wrote Assembly program for shift operations SHL, SHR, SAR, SAL.